

Extending Soft Start Time in TPS6107x Family of Boost Converters

Chris Glaser

PMP - Portable Power

ABSTRACT

In battery-powered equipment, extending the soft start time can be crucial to a glitch-free start-up. Especially toward the end of a battery's life, the voltage drop and increasing impedance of the battery from excessive inrush current into the power supply can be a problem. This application report demonstrates a simple circuit that extends the soft start time and reduces the inrush current on the TPS6107x family of boost converters.

Contents

1	TPS6107x Soft Start Operation.....	2
2	Extending the Soft Start Time.....	2
3	Setting the Soft Start Time	4
4	Transient Response	5
5	Inrush Current Reduction	6
6	Conclusion.....	7

List of Figures

1	TPS61070EVM With Added Soft Start Circuit	2
2	TPS61070EVM Soft Starting Into 50-Ω Load – 743-μs Soft Start Time.....	3
3	TPS61070EVM Soft Starting Into 50-Ω Load with C6=1000 pF and R3=162 kΩ – 971-μs Soft Start Time	3
4	TPS61070EVM Soft Starting Into 50-Ω Load with C6=1800 pF and R3=162 kΩ – 1.379-ms Soft Start Time	4
5	TPS61070EVM Transient Response Without Soft Start Circuit	5
6	TPS61070EVM Transient Response With Soft Start Circuit (C6=1800 pF, R3=162 kΩ) .	5
7	TPS61070EVM Start-up Powered From Two AA Batteries Without Soft Start Circuit	6
8	TPS61070EVM Start-up Powered From Two AA Batteries With Soft Start Circuit (C6=1800 pF, R3=162 kΩ)	6

List of Tables

1	Soft Start Times and Inrush Currents of the TPS61070EVM With Different Values of C6 and R3	4
---	--	---

1 TPS6107x Soft Start Operation

The TPS6107x has three cycles or phases of soft start:

- Cycle 1 (Precharge) charges the output capacitors to the input voltage. The internal synchronous FET operates in the linear region and delivers a DC, fixed current to the output capacitor during this phase, as shown in Figure 22 in the data sheet ([SLVS510](#)). The TPS6107x enters cycle 1 when enabled and V_{in} is above the undervoltage lockout. It exits cycle 1 after charging the output voltage up to a value that is almost equal to the input voltage.
- Cycle 2 (Fixed Duty Cycle Control) operates after cycle 1 ends. During cycle 2, the TPS6107x switches with a fixed 70% duty cycle. The TPS6107x enters cycle 2 when the cycle 1 is complete and the output voltage is less than 1.8 V. If the output voltage is greater than 1.8 V at the end of cycle 1, then cycle 2 is skipped. The TPS6107x only leaves cycle 2 when the output voltage is greater than 1.8 V.
- Cycle 3 (Reduced Current Limit) starts normal boost converter operation. During the third cycle of soft start, the error amplifier takes over and switches at the proper duty cycle, based on input and output voltage. During this cycle, the current limit is reduced to 50% of the nominal current limit to minimize inrush current. The TPS6107x enters cycle 3 directly from cycle 1 when the input voltage is greater than 1.8 V. It enters cycle 3 directly from cycle 2 when the input voltage is less than 1.8 V. The TPS6107x leaves cycle 3 and begins normal operation with the standard current limit when the output capacitor charges to the nominal output voltage.

2 Extending the Soft Start Time

The technique used in this application report to extend the soft start time adds an RC circuit connected through a diode to the FB pin. [Figure 1](#) shows the TPS61070EVM with the added soft start circuit (C6, R3, and D1). By feeding a current onto R2 through C6 and D1, the error amplifier reacts as if the output voltage is higher than it actually is and reduces the duty cycle accordingly. Thus, the output voltage increases more slowly. As the output voltage comes into regulation, C6 charges up and becomes more and more of an open circuit, while R3 pulls the remaining charge to ground. Thus, soft start is ended and the error amplifier regulates the output voltage to the proper level.

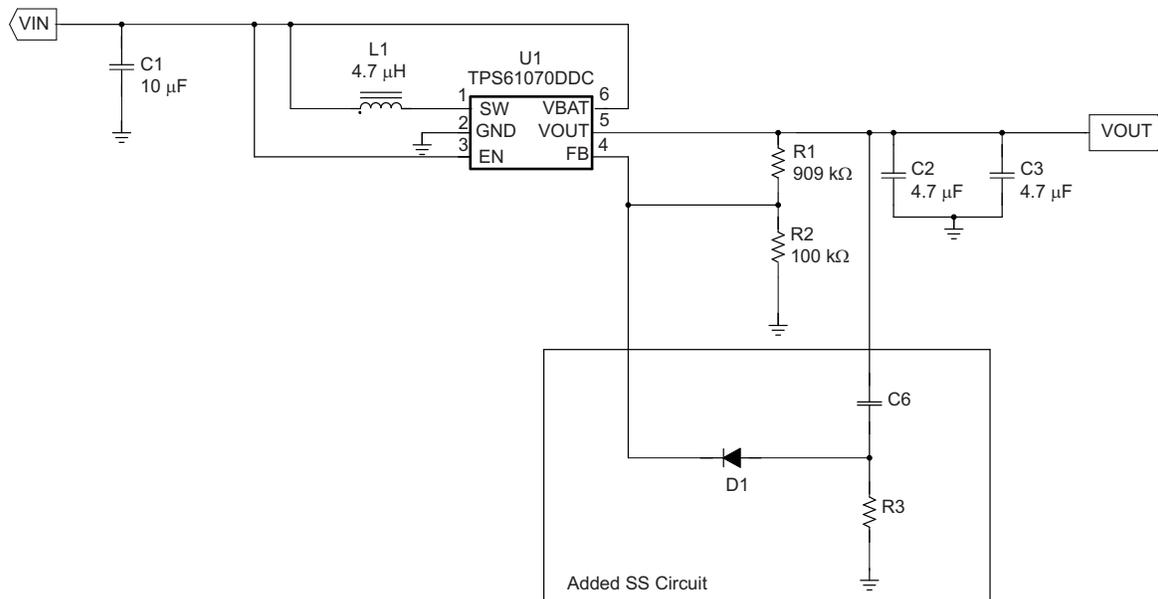


Figure 1. TPS61070EVM With Added Soft Start Circuit

[Figure 2](#) shows the TPS61070EVM starting into a 50-Ω load with 3.6-V input voltage. [Figure 3](#) and [Figure 4](#) show the same EVM and load conditions but the soft start circuit has been added. The diode used in these tests was a 1N4148.

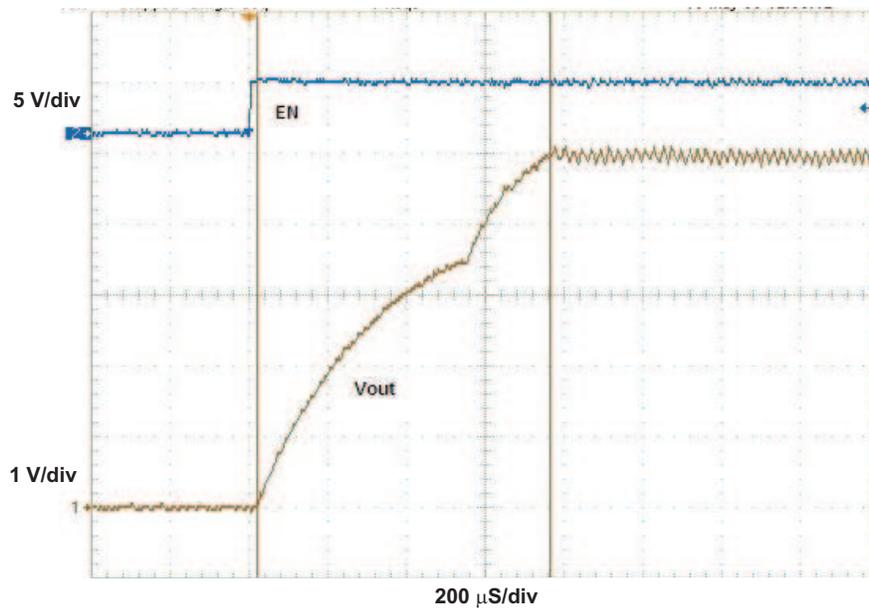


Figure 2. TPS61070EVM Soft Starting Into 50-Ω Load – 743-μs Soft Start Time

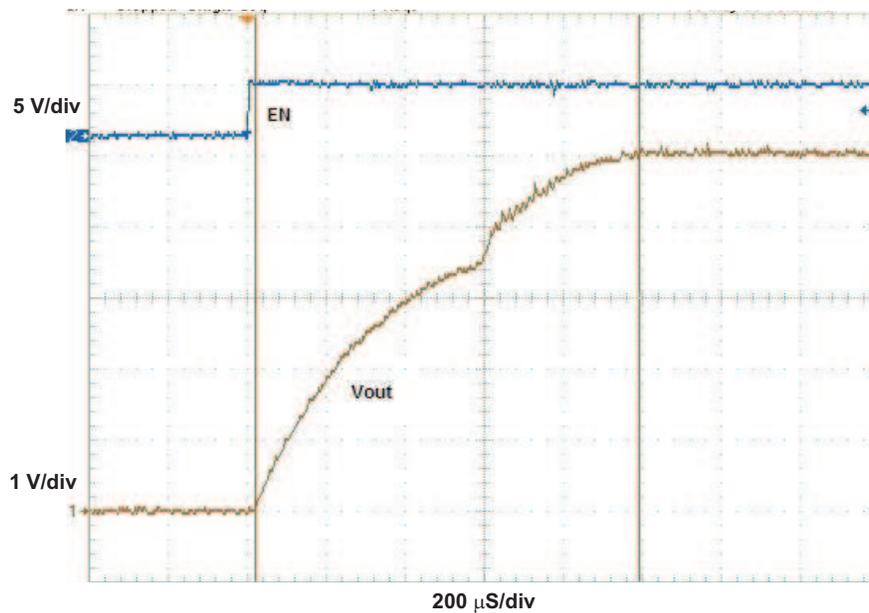


Figure 3. TPS61070EVM Soft Starting Into 50-Ω Load with C6=1000 pF and R3=162 kΩ – 971-μs Soft Start Time

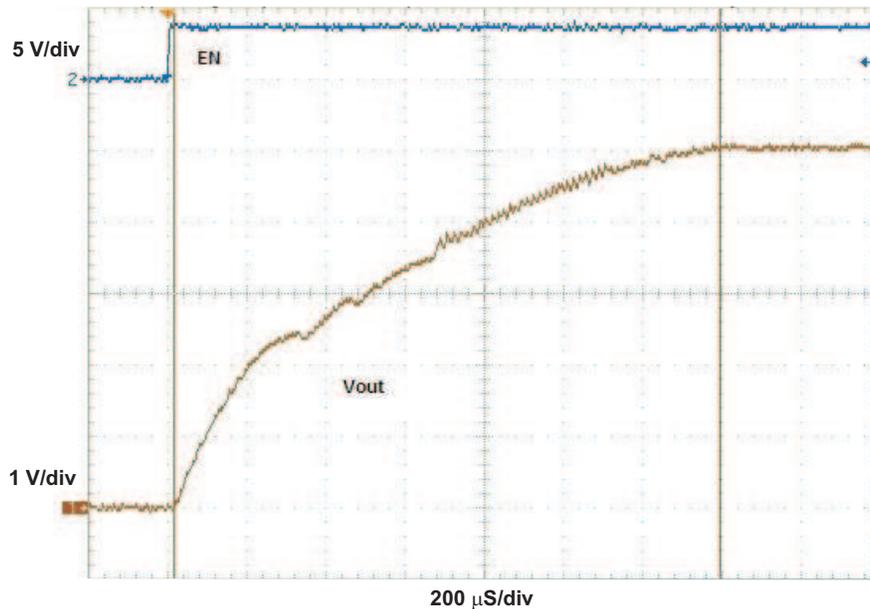


Figure 4. TPS61070EVM Soft Starting Into 50-Ω Load with C6=1800 pF and R3=162 kΩ – 1.379-ms Soft Start Time

3 Setting the Soft Start Time

The soft start time is roughly proportional to the product of R3 and C6. As this product goes up, the soft start time increases and the inrush current is reduced. If the product is too low, hardly any soft start time is added. Note that the allowable inrush current during the first cycle of soft start [Figure 22 in the TPS61070 data sheet ([SLVS510](#))] cannot be reduced.

[Table 1](#) shows measured soft start times with various values of R3 and C6. The amount of output capacitance and expected load during startup are also critical factors in determining the soft start time for a particular application. [Table 1](#) must be used as a guide to selecting R3 and C6. Laboratory verification is necessary to ensure a particular soft start time for a given system with a given output capacitance and load in the midst of component variation over tolerance and temperature.

Table 1. Soft Start Times and Inrush Currents of the TPS61070EVM With Different Values of C6 and R3

R3 (Ω)	C6 (nF)	Soft Start Time ⁽¹⁾ (ms)	Peak Inrush Current ⁽²⁾ (mA)
10k	1.8	0.8	200
10k	15	1.1	120
10k	47	3.2	100
10k	100	6.4	100
10k	150	9.5	100
162k	1	1.0	120
162k	1.8	1.4	100
162k	4.7	3.8	100
162k	10	7.8	100
162k	15	11.2	100

⁽¹⁾ Measured on the TPS61070EVM with 3.6V input and 50 Ω load

⁽²⁾ Measured on the TPS61070EVM with two depleted AA batteries (~2.1 V) and 500-Ω load

4 Transient Response

Because the small-signal model of the diode D1 is a small capacitor in parallel with a resistor, it is possible for this circuit to affect the control loop. One way to see if the loop is affected is to look at the response of the circuit to a load step and see if this response is changed significantly by the addition of the soft start circuitry.

Figure 5 and Figure 6 show the resulting output voltage deviation of the TPS61070EVM when subjected to a 20-mA to 180-mA load step. (Note: during light load (20 mA), the TPS61070 goes into PFM mode, so the output ripple is larger).

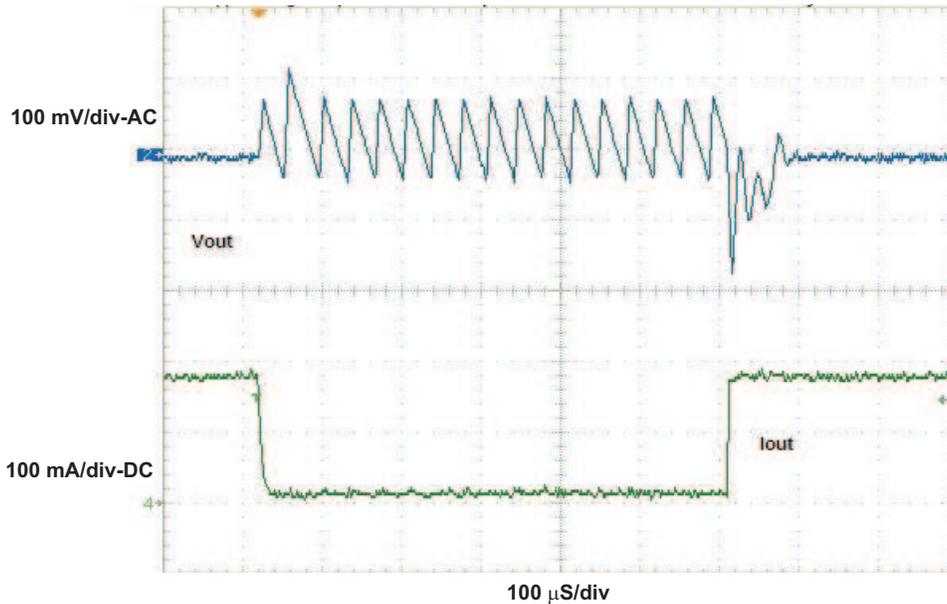


Figure 5. TPS61070EVM Transient Response Without Soft Start Circuit

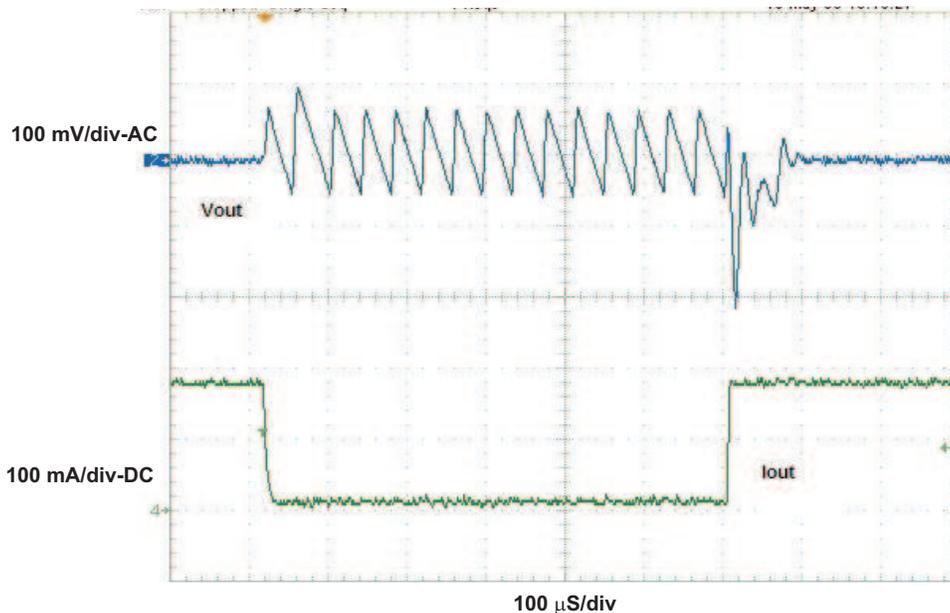


Figure 6. TPS61070EVM Transient Response With Soft Start Circuit (C6=1800 pF, R3=162 kΩ)

Because [Figure 5](#) and [Figure 6](#) are nearly identical; the added soft start circuit has not affected the control loop significantly.

5 Inrush Current Reduction

[Figure 7](#) and [Figure 8](#) demonstrate how the additional soft start circuitry reduces the sagging battery voltage caused by the large inrush current at turnon. Two AA batteries with a combined voltage of 2.1 V power the TPS61070EVM, which has a 500- Ω load. Without the soft start circuitry, the TPS61070 has an inrush current of 200 mA, which results in a battery voltage droop of 260 mV. With the soft start circuit, the inrush current is only 100 mA, which results in a 140-mV droop in battery voltage.

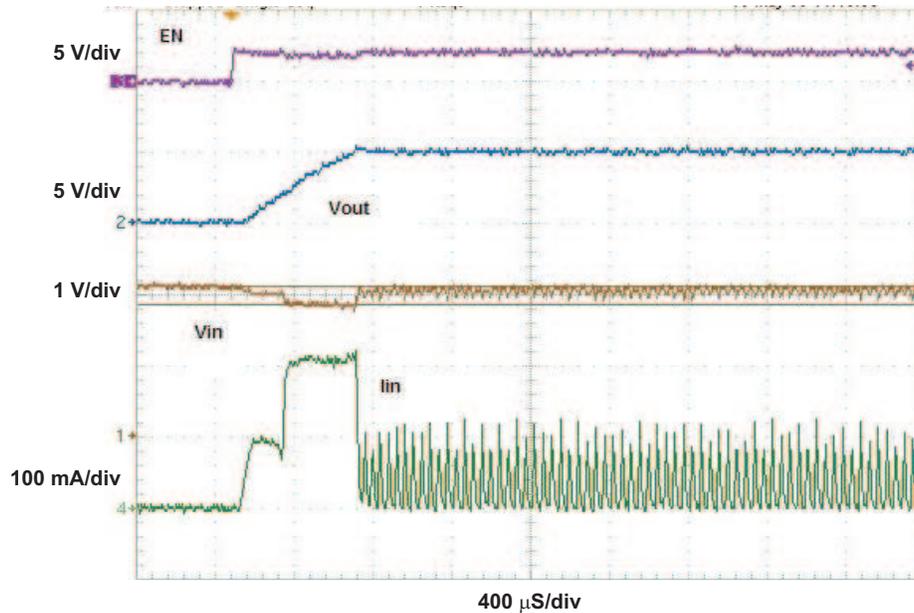


Figure 7. TPS61070EVM Start-up Powered From Two AA Batteries Without Soft Start Circuit

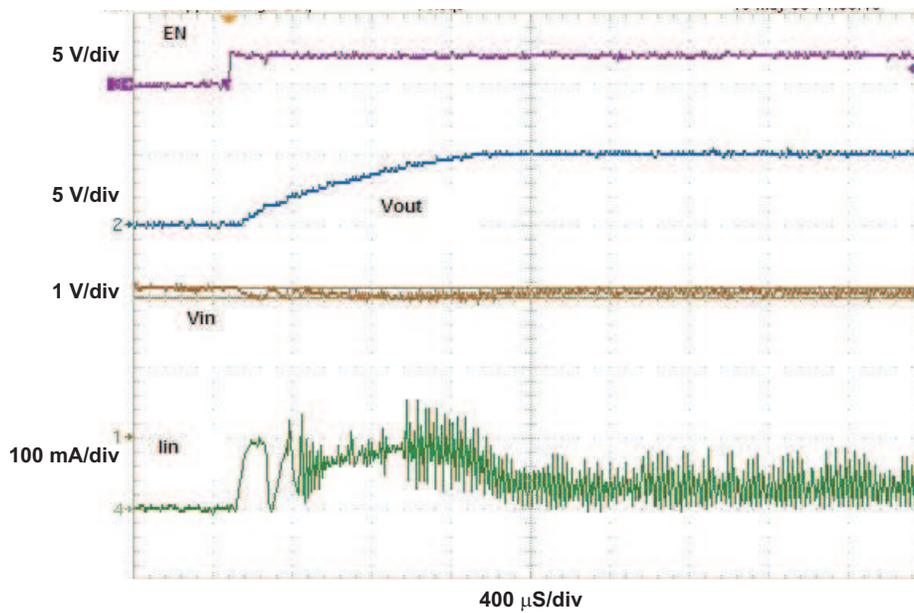


Figure 8. TPS61070EVM Start-up Powered From Two AA Batteries With Soft Start Circuit (C6=1800 pF, R3=162 k Ω)

6 Conclusion

This application report has demonstrated a simple circuit to extend the soft start time of the TPS6107x family of boost converters, while also reducing the inrush current drawn from a battery. The addition of a resistor, capacitor, and diode circuit creates a user-programmable soft start time that does not affect the control loop and thus does not affect the circuit's response to a load step.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated